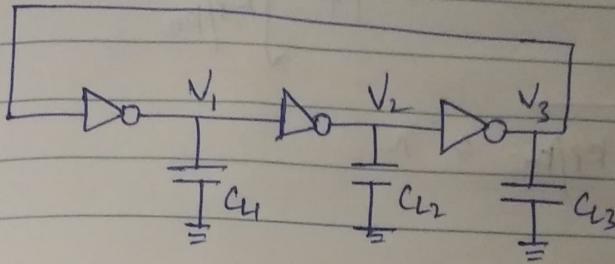


Assignment 10

Ans 1 :-)



each oscillator consist of N no. of rise delays ( $\tau_r$ )  
& N no. of fall delays ( $\tau_f$ )

total time :  $(\tau_r + \tau_f)_1 + (\tau_r + \tau_f)_2 + \dots + (\tau_r + \tau_f)_N$

If delay is same for each stage & transistor,

$$T = 2\tau \cdot N \quad \therefore F = 1/T = 1/2\tau N$$

b) if  $\tau$  depends on  $w$  &  $L$  & both  $w$  &  $L$  are scaled by  $s$ .

$$w' \rightarrow w/s$$

$$L' \rightarrow L/s$$

$$\frac{w'}{L'} = \frac{w/s}{L/s} = \frac{w}{L}$$

$\tau$  remains same.

*Aayush*

$$\underline{\text{Ans2.)}} \quad V_t = 2.2 = V_{th}n + (V_{DD} - V_{t,p}) \sqrt{\frac{k_p}{k_n}}$$

$$\underline{1 + \sqrt{\frac{k_p}{k_n}}}$$

$$\underline{2.2 \sqrt{\frac{k_p}{k_n}} = n}$$

$$\underline{2.2 = 0.8 + \frac{(5-1)n}{1+n}}$$

$$2.2 + 2.2n = 0.8 + 4n \Rightarrow n = 0.77$$

$$\frac{M_n C_{ox} (W/L)_p}{M_n C_{ox} (W/L)_n} = \frac{20}{50} = \frac{3}{5} \rightarrow W_p = 1.5 W_n$$

$$I_{avg} = \frac{1}{2} \left[ i_c (V_{in} = 0, V_{out} = 0.5) + i_c (V_{th} = 0, V_{out} = 4.5) \right]$$

$$\rightarrow V_{SD} - V_{t,p} \geq V_{SD}$$

$$V_{DD} - V_{t,p} \geq V_{DD} = V_{out}$$

$$\begin{aligned} &\rightarrow 4.5 - 0.5 \rightarrow \text{lin} \\ &\rightarrow 4 > 5 - 4.5 \rightarrow \text{sat} \end{aligned}$$

approx

$$I_{lin} = \frac{k_f}{2} \left[ 2(4)(0.5) - (0.5)^2 \right] = 1.875 k_f$$

$$I_{sat} = \frac{k_f}{2} [5-1]^2 = 8 k_f$$

$$I_{avg} = \frac{1}{2} [8 + 1.875] = \underline{4.94}$$

$$\therefore k_f = 20 \times 10^6 W_p$$

$$W_p = \frac{8 \times 10^{-12}}{\frac{5 \times 10^{-9} \times 4.94 \times 20 \times 10^{-6}}{8 \times 10 \times 10 \times 10}} = \underline{\underline{16.19}}$$

$$W_p = 1.5 W_n \rightarrow W_n = \frac{W_p}{1.5} = \frac{16.19}{1.5} = \underline{\underline{10.8}}$$

*aynabu*